

Verification of Thevenin's Theorem

Procedure:

Keep all the resistances (R_1, R_2, R_3, R_4) close to their respective maximum values. Choose any arbitrary values of V_1 and V_2 .

Experiment Part Select:

Case 1:
Select switch of S_1 to Power and S_2 to load. Simulate the program. Observe the result from Table 1.

Case-2:

a) **Thevenin Voltage analysis:**
Apply switch S_1 to power and S_2 to intermediate. Simulate the program. Read Thevenin voltage (V_{th}) from Case 2 tab.

b) Thevenin Resistance analysis:


Apply switch S_1 to short and S_2 to power. Simulate the program. Read Thevenin resistance (R_{th}) from Case 2 tab

Case-3: Using V_{th} and R_{th} determine Load Current:

Specify the load resistance in case of the result table as the same load resistance entered in the main circuit. Simulate the program. Read Load current (I_L) from Case 3 tab. Compare the load currents (I_L) obtained from above two cases.

MC-Moving Coil.

MC- Moving Coil.
DPDT- Double pole Double throw.
N.B.- All the resistances are in ohms

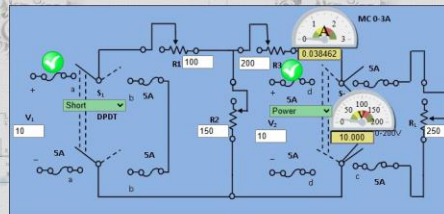


Case 1

Case 2(a)

Case 2(b)

Case 3

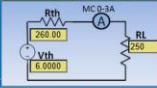Click on simulate to get the Load Current(I_L) from the Thevenin equivalent parameter of the above circuit.



Load Current(I_L) :

Load current(I_D):

Simulate

Fill data to the table

Observation Table:

Serial no. of Observation	Load Current(I_L) from case 1	Load Voltage(V_L)	Load Resistance (R_L)= V_L/I_L	Thevenin Voltage(V_{th}) from case 2(a)	2nd Voltage source(v) from case 2(b)	Ammeter Reading(I) from case 2(b)	Thevenin Resistance $R_{th}=V/I$	Load current (I_L)= $V_{th}/(R_{th}+R_L)$
---------------------------	-----------------------------------	-----------------------	--------------------------------------	---	--	---------------------------------------	----------------------------------	---